
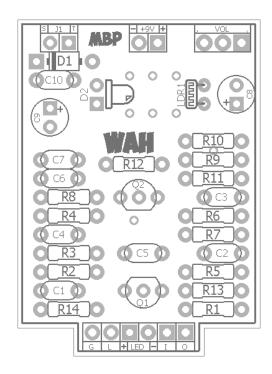


FX TYPE: Filter © 2016 madbeanpedals

1.3" W x 1.8" H

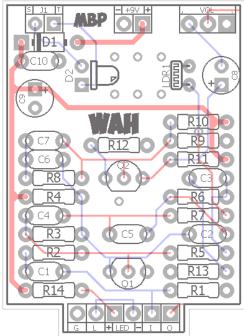



| B.O.M. | | | | | | |
|-----------|------|------|------|--------------------|---------|--|
| Resistors | | Caps | | Transistors | | |
| R1 | 1M | C1 | 100n | Q1, Q2 | 2N5088 | |
| R2 | 330k | C2 | 100n | Diodes | | |
| R3 | 4M7 | C3 | 15n | D1 | 1N5817 | |
| R4 | 10k | C4 | 2n2 | D2 | 3mm LED | |
| R5 | 180k | C5 | 6n8 | Photocell | | |
| R6 | 180k | C6 | 100n | LDR1 | 9203 | |
| R7 | 47R | C7 | 2n2 | Pot | | |
| R8 | 100k | C8 | 4u7 | VOL | 100kB | |
| R9 | 100k | C9 | 47uF | | | |
| R10 | 470k | C10 | 100n | | | |
| R11 | 10k | | | | | |
| R12 | 2k7 | | | | | |
| R13 | 33k | | | | | |
| R14 | 4k7 | | | | | |


| Shopping List | | | | | | | |
|---------------|-----|---------------------|----------|--|--|--|--|
| Value | QTY | Туре | Rating | | | | |
| 47R | 1 | Metal / Carbon Film | 1/4W | | | | |
| 2k7 | 1 | Metal / Carbon Film | 1/4W | | | | |
| 4k7 | 1 | Metal / Carbon Film | 1/4W | | | | |
| 10k | 2 | Metal / Carbon Film | 1/4W | | | | |
| 33k | 1 | Metal / Carbon Film | 1/4W | | | | |
| 100k | 2 | Metal / Carbon Film | 1/4W | | | | |
| 180k | 2 | Metal / Carbon Film | 1/4W | | | | |
| 330k | 1 | Metal / Carbon Film | 1/4W | | | | |
| 470k | 1 | Metal / Carbon Film | 1/4W | | | | |
| 1M | 1 | Metal / Carbon Film | 1/4W | | | | |
| 4M7 | 1 | Metal / Carbon Film | 1/4W | | | | |
| 2n2 | 2 | Film | 16v min. | | | | |
| 6n8 | 1 | Film | 16v min. | | | | |
| 15n | 1 | Film | 16v min. | | | | |
| 100n | 4 | Film | 16v min. | | | | |
| 4u7 | 1 | Electrolytic | 16v min. | | | | |
| 47uF | 1 | Electrolytic | 16v min. | | | | |
| 2N5088 | 2 | | | | | | |
| 1N5817 | 1 | | | | | | |
| LED | 1 | Red, Diffused | 3mm | | | | |
| Photocell | 1 | 9203 | | | | | |
| 100kB | 1 | PCB Mount | 9mm | | | | |

Note – Be sure to use low profile electrolytic caps in all 1590A builds (5 to 7mm height max)

9203 photocell: http://smallbear-electronics.mybigcommerce.com/photocells-cds-5mm-diameter/9mm Pot: http://smallbear-electronics.mybigcommerce.com/alpha-single-gang-9mm-pc-mount/

1590A Drill Guide

3.63"W x 5.72"H

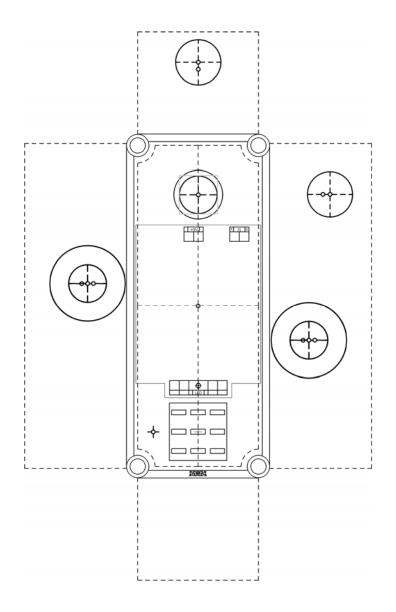

Download the Photoshop drill template: http://www.madbeanpedals.com/projects/Tapanatorator/Tapanator DRILL.zip

Overview

The Wah project is designed exclusively for the Tapanatorator controller. It is based on the Colorsound Inductorless and is similar to the wah implementation in the MBP Dig Dug2 project.

There is only one control for the Wah - a volume. You can alter the corner frequency of the wah by adjusting the LED brightness on the Tapanator (T1-T3 on the controller unit).

A 9203 photocell is indicated for all the Tapanatorator projects. A VTL5C3 will also work. However, the 9203 is much cheaper than using a pre-made vactrol.

