
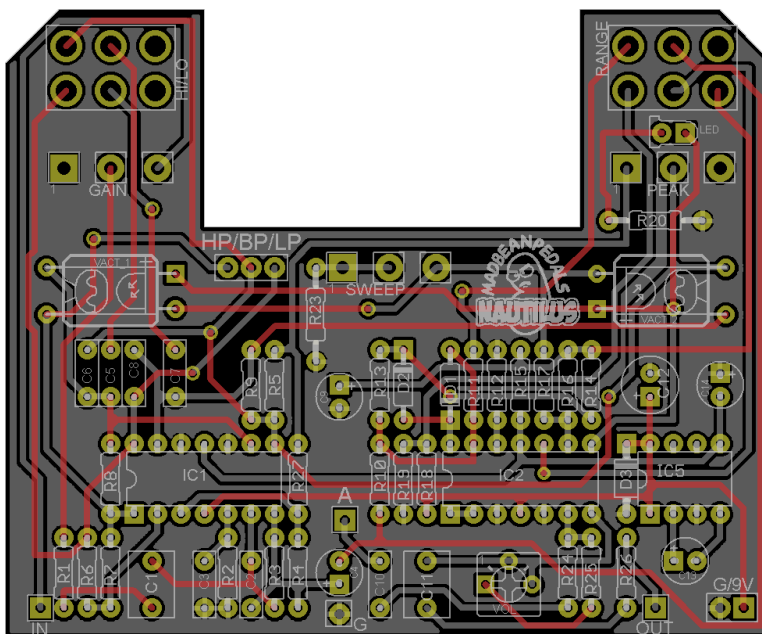


NAUTILUS

fx type: filter

© 2012 [madbeanpedals](http://madbeanpedals.com)

3.275" W x 2.675" H

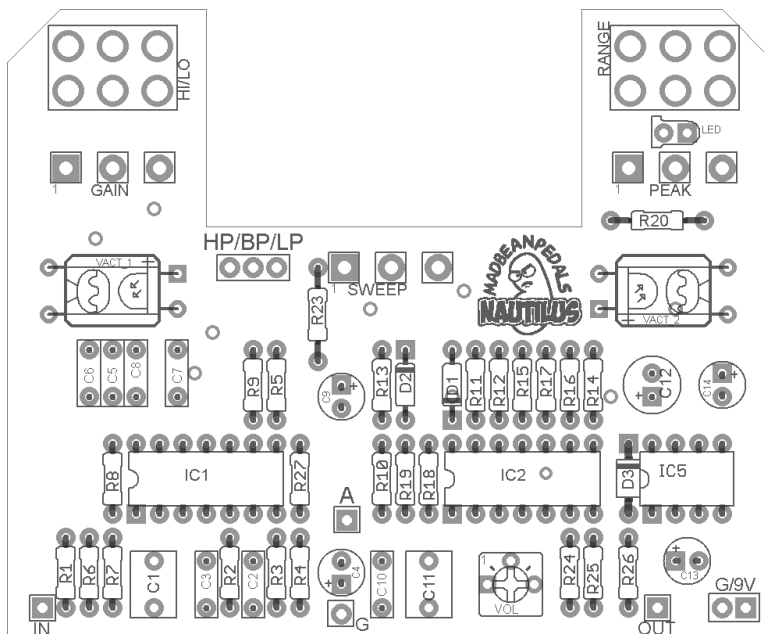

Nautilus PCBs purchased from madbeanpedals (or etched from the included PCB artwork) may be used for small quantities of commercial pedal building (bulk discounting on PCBs is not offered). You may not, however, offer these PCBs for commercial resale (re-distribution) or as part of a "kit". Selling and trading through DIY forums is, as always, completely legit.

www.madbeanpedals.com
BUILD.SHARE.LEARN

B.O.M.

Resistors		Caps		P4T	
R1	3k3	C1	1uF	D1, D2	1N914
R2	120k	C2	10pF	D3	1N4001
R3	120k	C3	100n	LED	LED3MM
R4	4k7	C4	2u2	ICs	
R5	390k	C5	2n2	IC1, IC2	TL074
R6	22k	C6	1n8	IC5	TC1044SCPA
R7	22k	C7	2n2	Vactrols	
R8	220k	C8	1n8	VACT_1, 2	see notes
R9	220k	C9	4u7	Switches	
R10	22k	C10	220n	RANGE	DPDT On/On
R11	12k	C11	1uF	HI/LO	DPDT On/On
R12	1M	C12	220uF	MODE	3P4T
R13	1M	C13	10uF	Trimpot	
R14	330R	C14	10uF	VOL	50k
R15	47k			Pots	
R16	120k			PEAK	250kB
R17	120k			GAIN	1MA
R18	180k			SWEEP	5kB
R19	120k				
R20	1k5				
R23	330R				
R24	10k				
R25	10k				
R26	560R				
R27	12k				

Overview

The **Nautilus** is a heavily modified and “modernized” Mutron III; a venerated classic of funk, jam and many other styles of music. The effect is an envelope driven filter with many choices for shaping and refining both how the filter behaves and how it interacts with your guitar dynamics.

The **Nautilus** implements several changes to the original design to accommodate more modern building techniques, as well as part availability. These include:

- True-Bypass operation
- Use of low-noise quad op-amps
- Use of two common vactrols in place of the custom-made dual vac in the original
- Output gain stage
- “Sweep” control
- Bi-polar supply via a common charge pump set-up

- Controls -

- **Gain** – The input gain of the filter effect. This drives not only the filter portion, but also the envelope. As the control is turned up, more overdrive is produced and the envelope becomes more sensitive to dynamics.
- **Sweep** – This control follows directly from R.G. Keen's suggestion. It allows one to make small adjustments to the overall LED brightness in the envelope section. The LEDs are what drive the Vactrols which in turn produce the sweeping filter effect.
- **Peak** – Adjusts the intensity of the resonant peak of the filters.
- **Hi/Lo** – Selects between two sets of filters, high and low.
- **Up/Down** – Selects two different modes for the LED drivers. The Up setting drives the LEDs from dark to light and the Down setting is the opposite.
- **Mode** – Selects three different filter types. HP is high-pass, LP is low-pass and BP is band-pass.
- **Vol** – This trimmer allows you to select the output gain of the effect. It will normally be set full counter-clockwise, but can be adjusted should you experience volume loss when the effect is turned on.

- Links -

[Musictronics Mutron III on discofreq.com](http://discofreq.com)

[Technology of Envelope-Controlled Filters on geofex.com](http://geofex.com)

Notes

The original Mutron used a custom made dual Vactrol which is no longer available. The Vactrol consisted of two photocells, one for each filter stage, and an LED driver in a cylindrical case. The **Nautilus** uses two Vactrol divers so there are two photocells, but one LED per photocell. It is imperative that you use the correct Vactrol for this build, otherwise it will not work.

You should use either the Macron MI1210CLF-R: <http://www.smallbearelec.com/servlet/Detail?no=1255>

or, the VTL5C3: <http://www.smallbearelec.com/servlet/Detail?no=347>

If you are unable to get either of these, then roll your own Vactrol using an LED and photocell with specs as close to 20-50k light, 10M dark. The closest match for this is the 9203 photocell listed here: <http://www.smallbearelec.com/servlet/Detail?no=711>

Do not expect that grabbing a couple of photocells out of the ol' Tayda bag is going to cut it...it won't! For the two LEDs, water clear 3mm or 5mm should be fine.

The other LED on the PCB is tied to the envelope filter. It will light up when the effect is engaged to give you visual feedback on how the envelope is behaving. If you wish to have an indicator LED for bypass, you should wire that separately to your 3PDT (see wiring diagram below).

You must use either the MX1044SCPA, TC1044SCPA or the ICL7660SCPA for IC5. Use only the "SCPA" designation...not the "CPA".


The Mutron used a 150kB pot for the Peak control. This is no longer a common value, so the **Nautilus** uses a 250kB pot with a resistor in parallel to approximate 150k. If you happen to have a 150k pot use that, but make sure to leave the resistor off (R5).

You can use 16mm short-pin PCB mounted pots for the three potentiometers.

The Sweep control is subtle, but will offer some variation in the swept filter by changing the max brightness of the two driver LEDs in the Vactrols. I've found that about 1/3rd up is the sweet spot.


You will likely find the Gain control quite sensitive in the last quarter of its range for *some* settings on the **Nautilus**. You can alter its response by changing to a different taper such as linear or reverse audio (people do seem to prefer a 1MC here).

Wiring

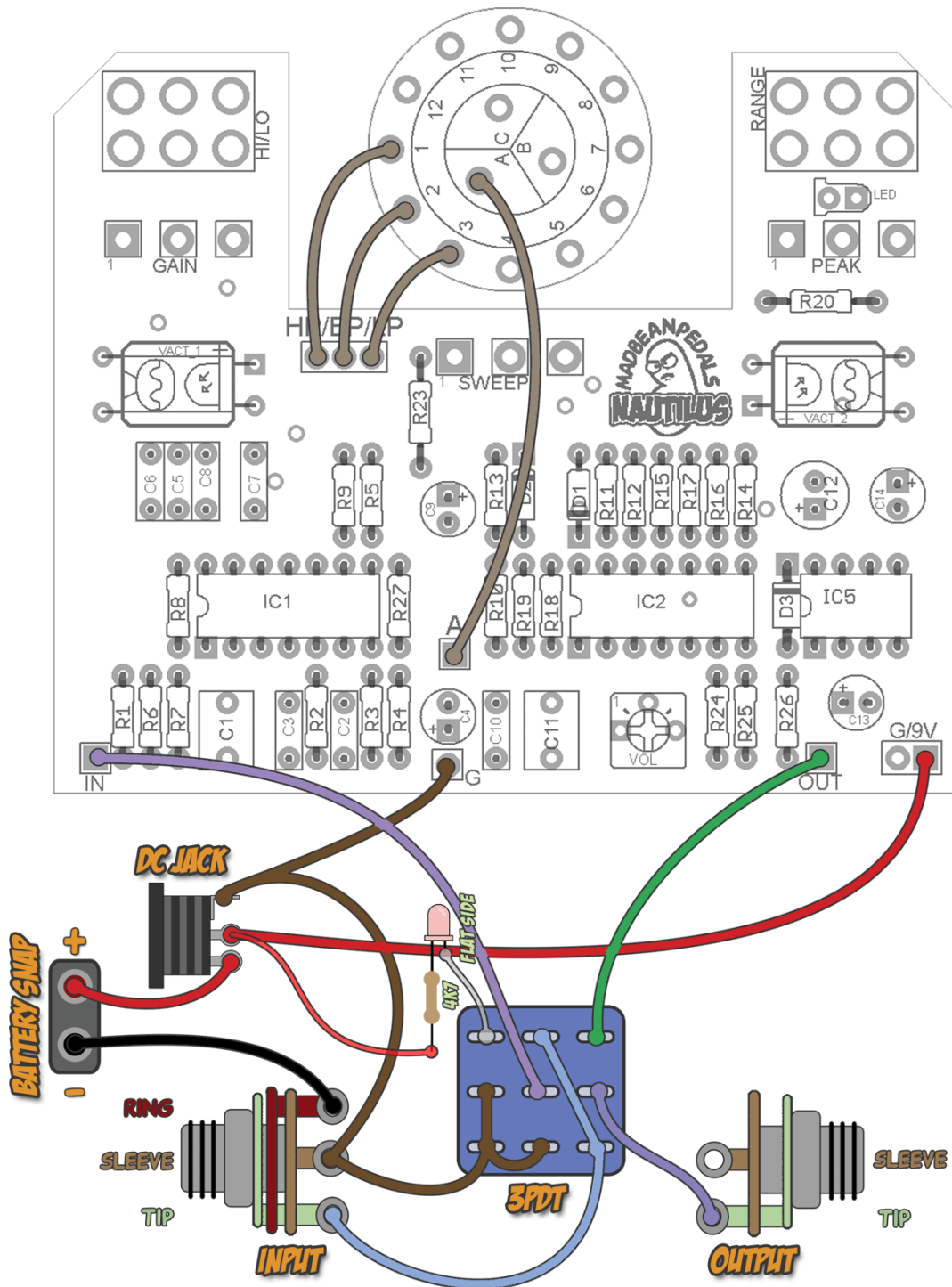


Drill Guide - 1590BB

5.81" W x 6.67" H

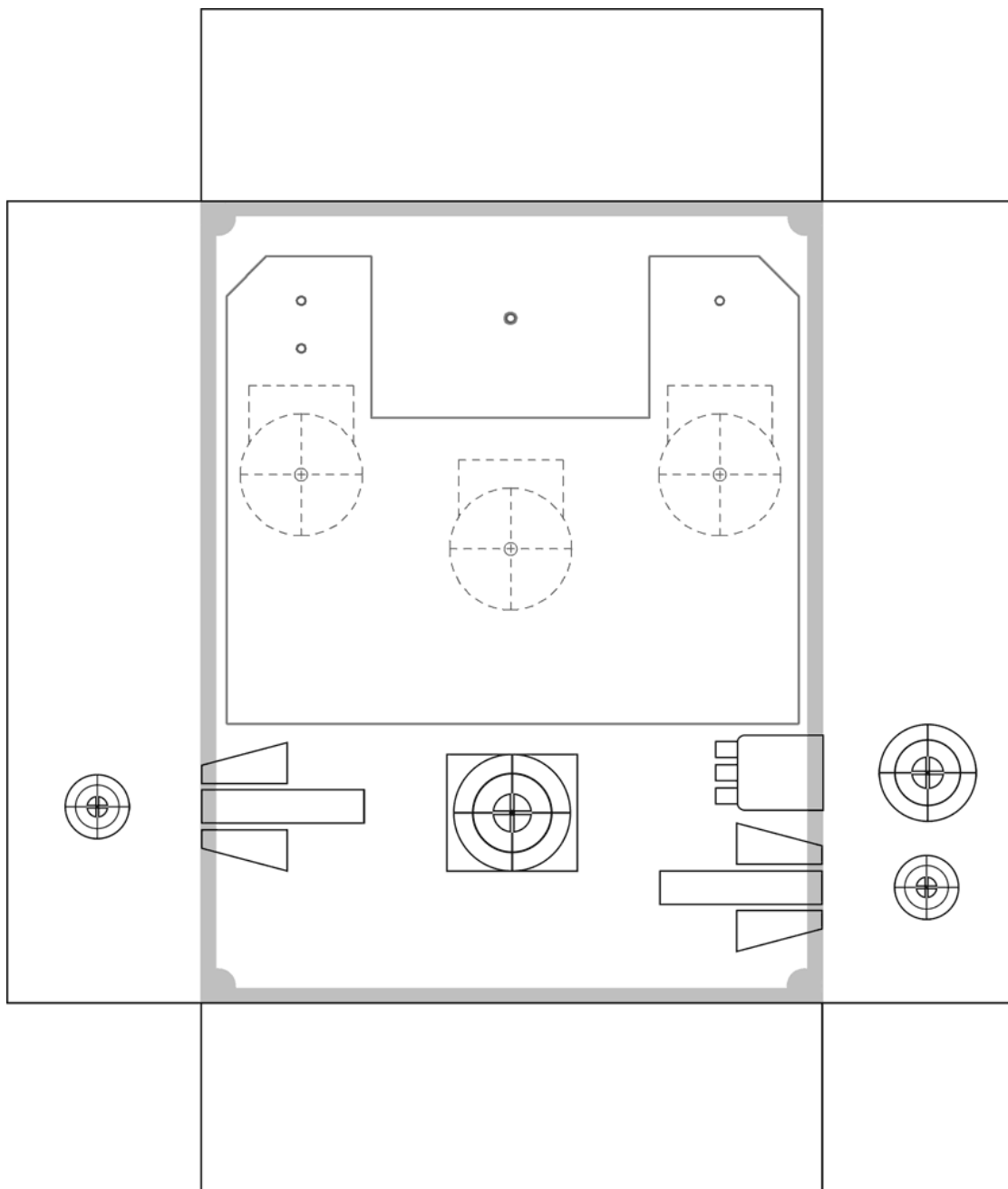


This template is approximate. Please check carefully before committing to drill!

Single Sided Artwork

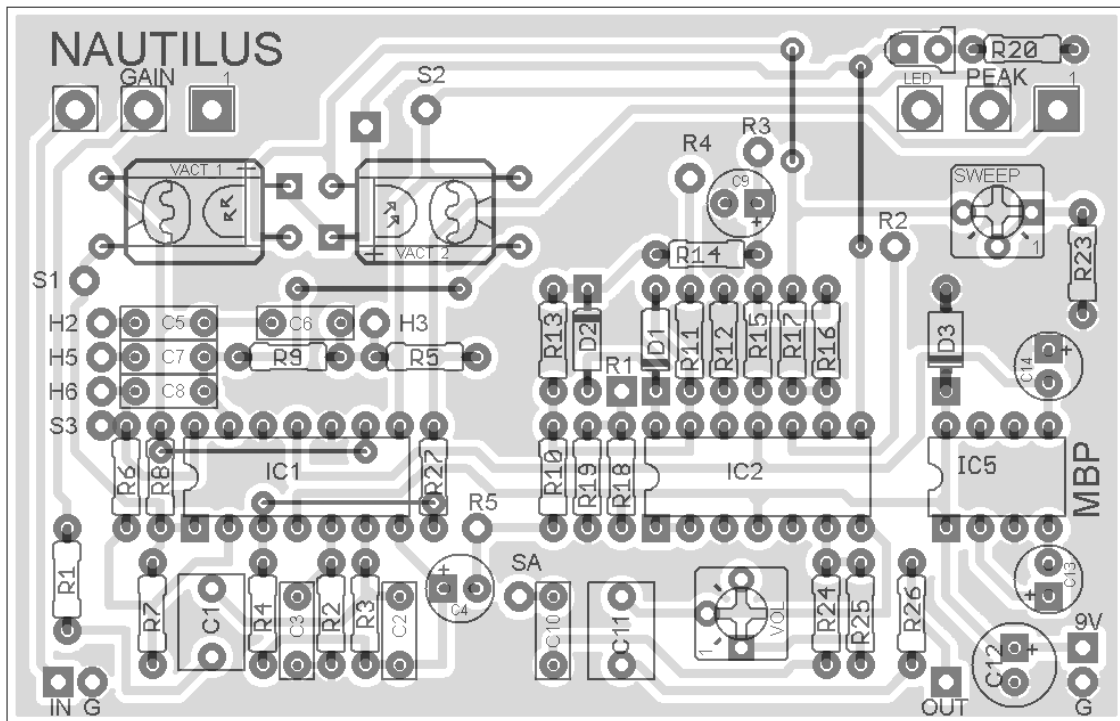


3.31" W x 2.14" H (inc. borders)

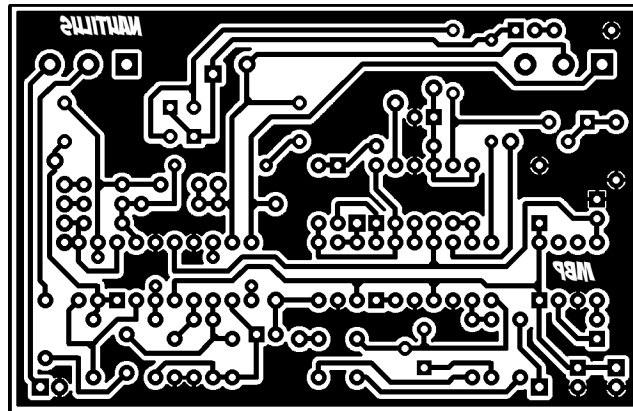


- There are 5 jumpers on this layout.
- You can use either a trimpot or regular pot for the Sweep control.
- You can use 16mm short-pin PCB mounted pots for the Gain and Peak controls.

Wiring – Single Sided

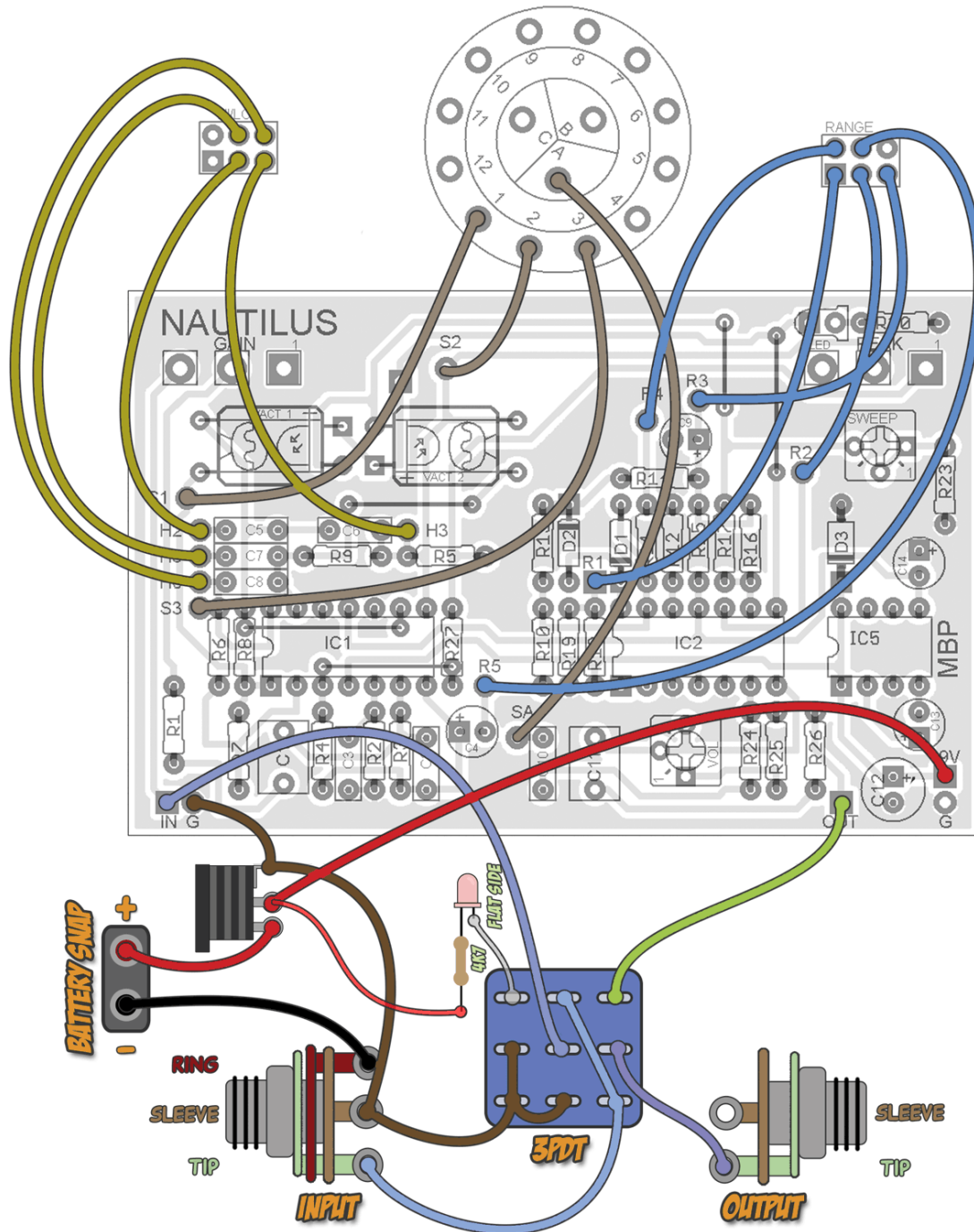

Drill Guide - Single Sided

5.81" W x 6.67" H

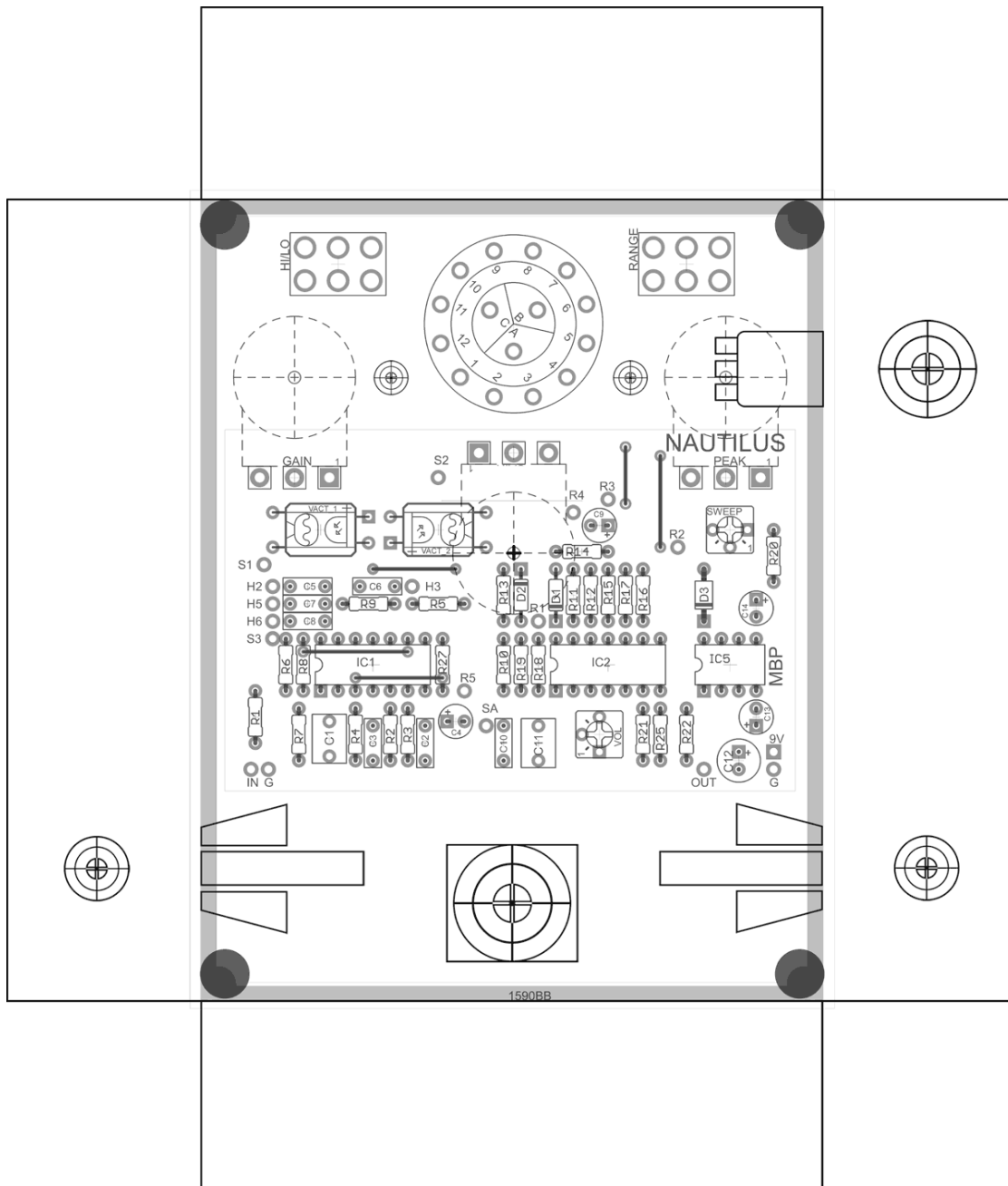

This template is approximate. Please check carefully before committing to drill!