

Smoothie

FX Type: **MODULATION**
Build Level: Intermediate
Based On: MXR® Phase45™

Last Updated: June 7, 2024 11:35 AM

© 2024 [madbeanpedals](#)



Overview

The **Smoothie** is based on the classic MXR® Phase 45™, which is a two stage phaser driven by simple LFO. The input is fed through a filter network and controlled resistively by two JFET transistors. The dry and wet signals are then mixed via R16/17 just before the output. This is the perfect phaser pedal for slow, subtle tone enhancement or fast but gentle swirls.

To learn more about how phasers function, please refer to [“The Technology of Phase Shifters and Flangers”](#) by R.G. Keen.

This project requires two matched JFET transistors. See the Build Notes for more details.

Controls


- **SPEED:** Modulation rate.
- **VOICE:** Selects between the stock phase caps and an alternate “univibe” set.

Terms of Use: You are free to use purchased **Smoothie** circuit boards for both DIY and small commercial operations. You may not offer **Smoothie** PCBs for resale or as part of a “kit” in a commercial fashion. Peer to peer re-sale is fine, though.


Technical assistance for is available via the [madbeanpedals forum](#). Please go there rather than emailing me for personal assistance. This is because (1) I'm not always available to respond via email in a timely and continuous manner, and (2) posting technical problems and solutions in the forum creates a record from which other members may benefit.

All copyrights and registered trademarks are property of their original owners. Any mention of trademarked or intellectual properties in this documents is purely for comparative purposes.


Parts Layout

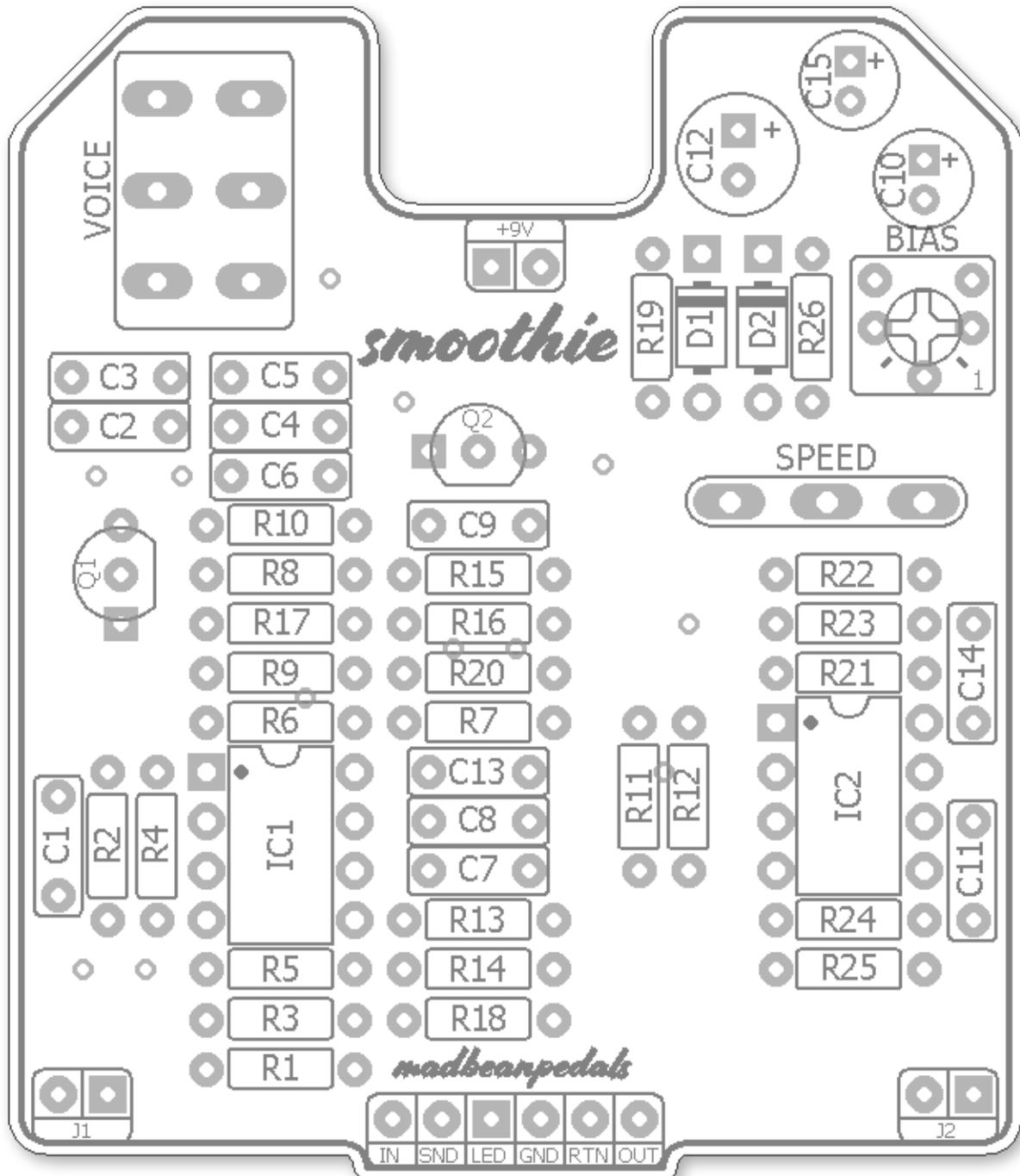


Component Values

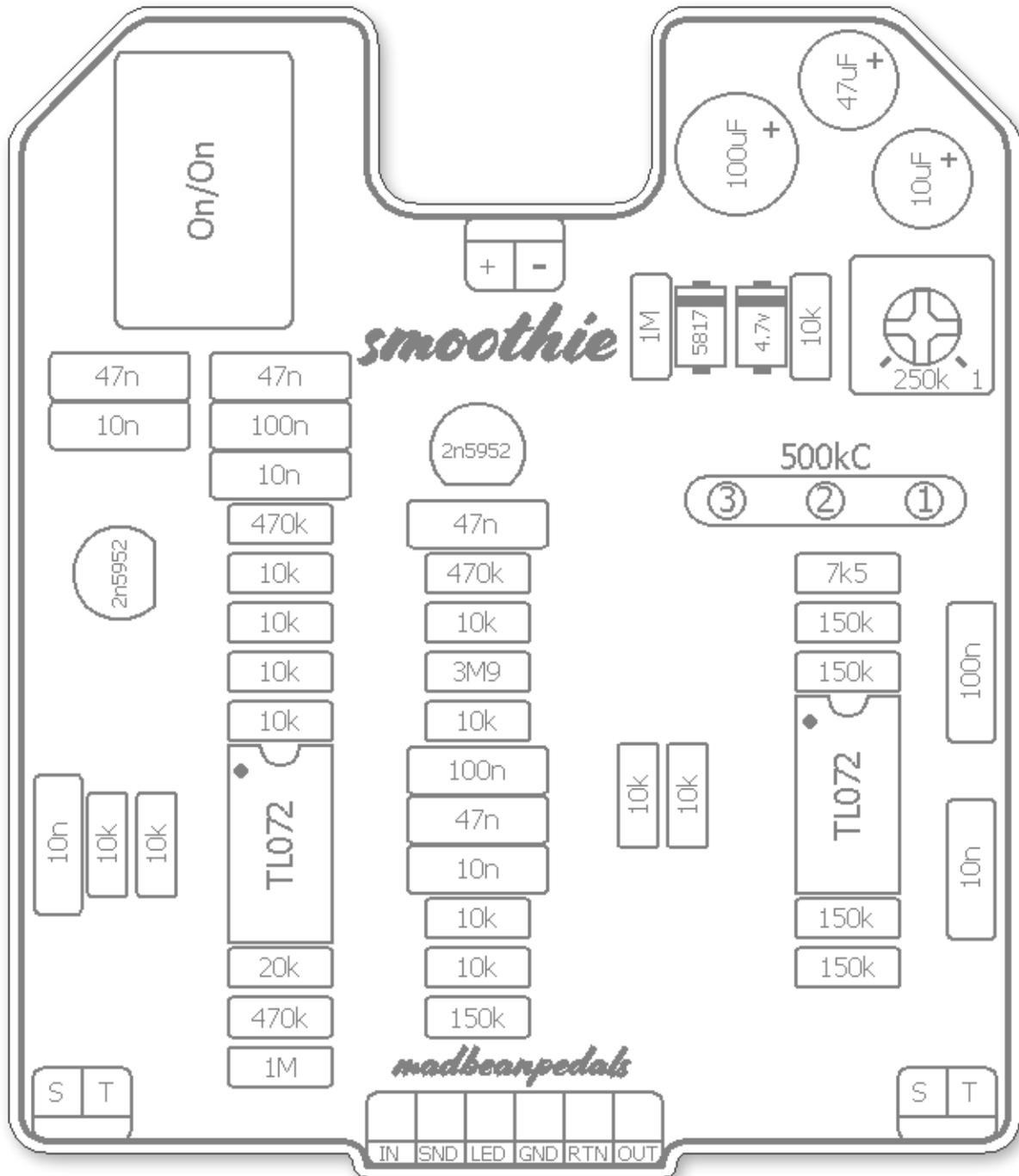

Trace Layout

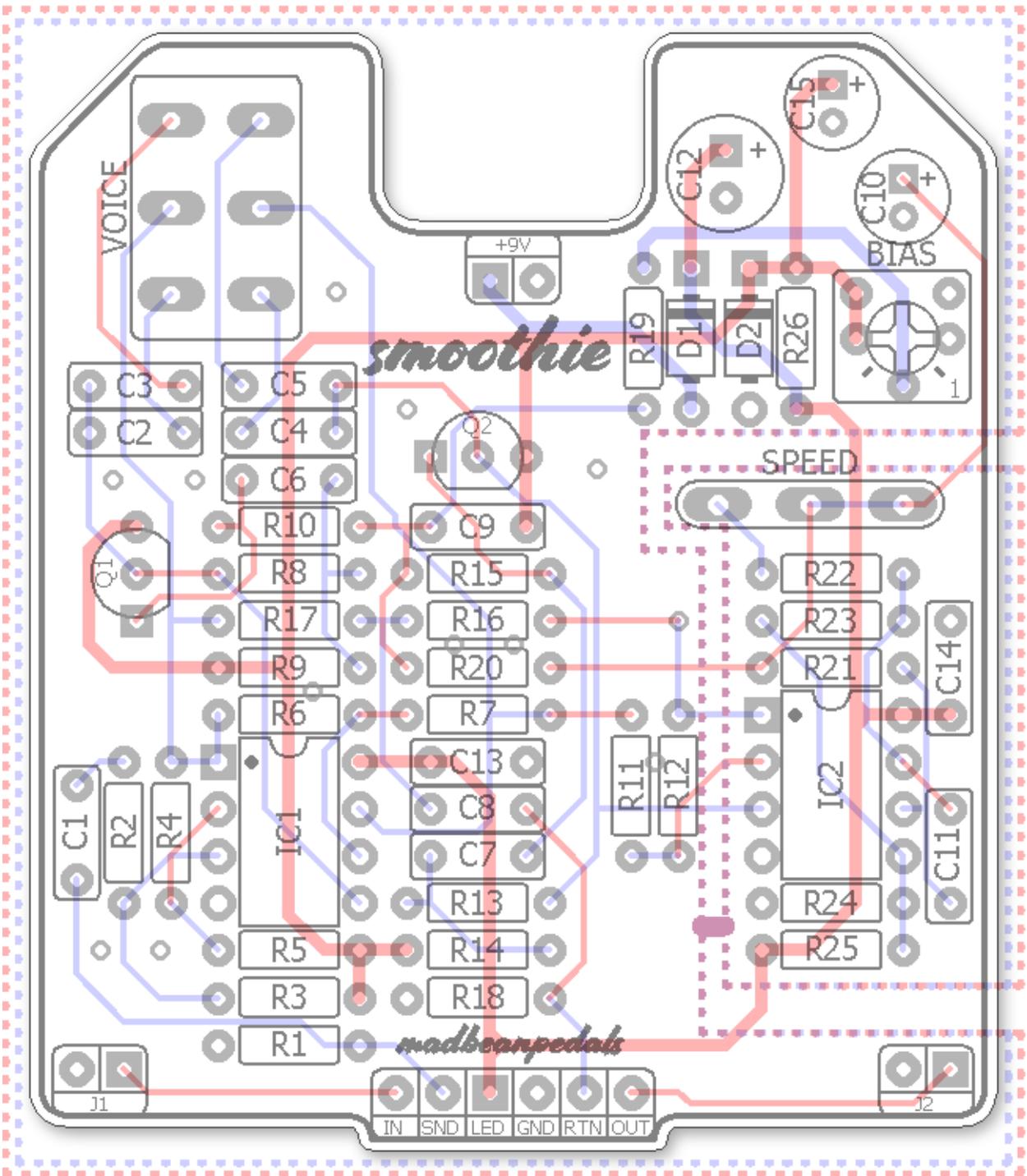

Wiring

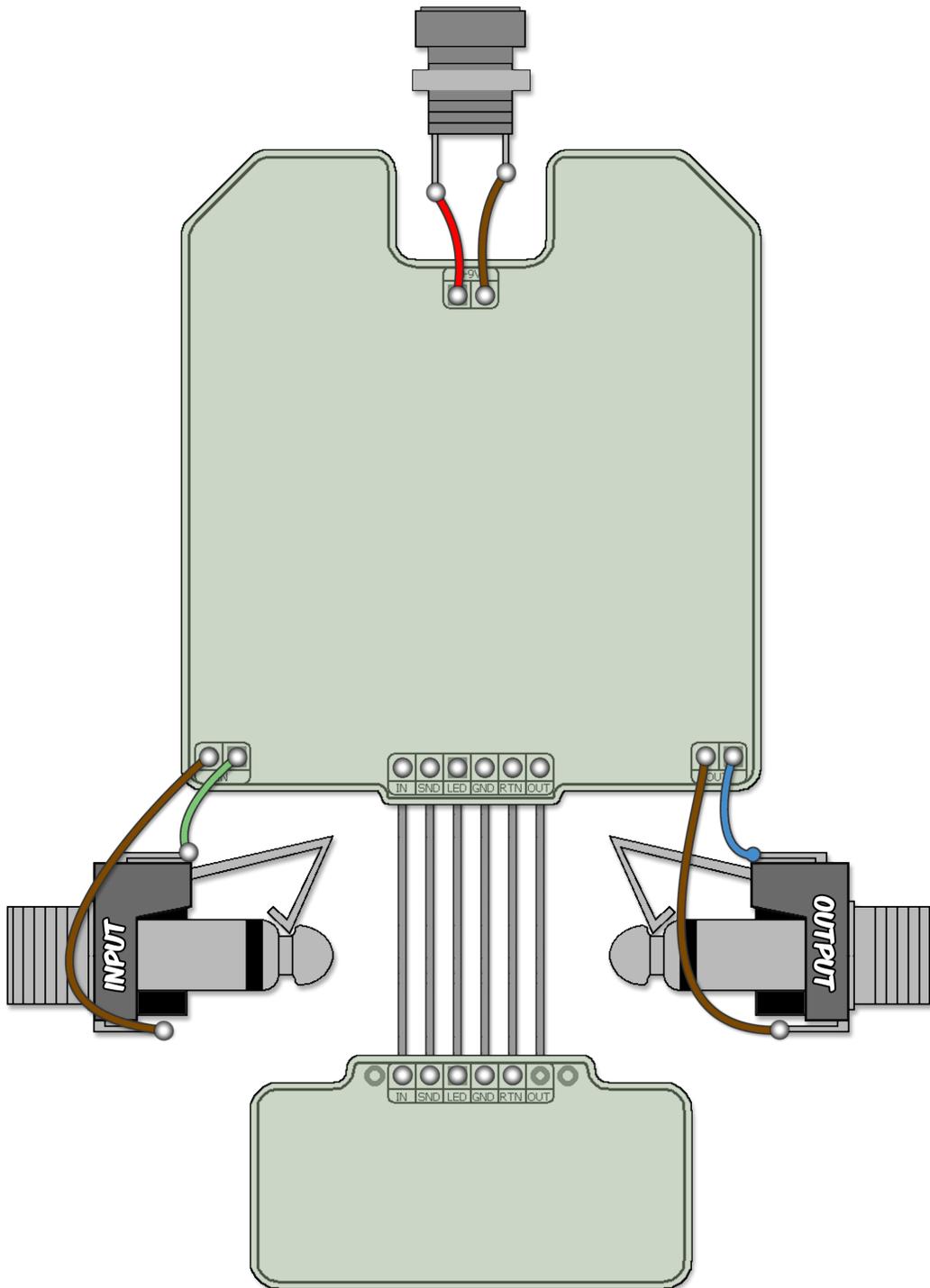

Unless otherwise noted, all Standard Series projects have the same wiring regardless of which 3PDT bypass board is used. A 6-pin, 2" ribbon cable is recommended for soldering the connections between the two PCBs.

B.O.M.

Resistors		Caps		Diodes	
R1	1M	C1	10n	D1	1n5817
R2	10k	C2	10n	D2	4.7v Zener
R3	470k	C3	47n	Transistors	
R4	10k	C4	100n	Q1	2n5952
R5	20k	C5	47n	Q2	2n5952
R6	10k	C6	10n	IC	
R7	10k	C7	10n	IC1	TL072
R8	10k	C8	47n	IC2	TL072
R9	10k	C9	47n	Switch	
R10	470k	C10	10uF	VOICE	On/On
R11	10k	C11	10n	Trimmer	
R12	10k	C12	100uF	BIAS	250k
R13	10k	C13	100n	Pot	
R14	10k	C14	100n	SPEED	500kC
R15	470k	C15	47uF		
R16	10k				
R17	10k				
R18	150k				
R19	1M				
R20	3M9				
R21	150k				
R22	7k5				
R23	150k				
R24	150k				
R25	150k				
R26	10k				

Shopping List

Value	QTY	Type	Rating
7k5	1	Carbon / Metal Film	1/4W
10k	13	Carbon / Metal Film	1/4W
20k	1	Carbon / Metal Film	1/4W
150k	5	Carbon / Metal Film	1/4W
470k	3	Carbon / Metal Film	1/4W
1M	2	Carbon / Metal Film	1/4W
3M9	1	Carbon / Metal Film	1/4W
10n	5	Film	16v min.
47n	4	Film	16v min.
100n	3	Film	16v min.
10uF	1	Electrolytic	16v min.
47uF	1	Electrolytic	16v min.
100uF	1	Electrolytic	16v min.
1n5817	1		
Zener	1	4.7v	1W
2n5952	2	matched	
TL072	2		
DPDT	1	On/On, Solder Lug or Pin Mount	
250k	1	Bourns 3362p or 6mm	
500kC	1	PCB Right Angle	16mm


Additional Hardware

- (1) 1590B enclosure
- (2) Lumberg 1/4" Compact mono jacks
- (1) Slim 2.1mm DC jack
- (1) Standard 3PDT footswitch
- (1) 5mm LED

Build Notes

Transistors

- The Smoothie requires the 2n5952 transistors to be matched for the phaser effect to work properly. While you may be able to stick a couple of random JFETS in there and get lucky, the best result comes from matching the cutoff voltages for the transistors as closely as possible. This is easy to do, provided you have a quantity of transistors available to work with.
- The process involves placing individual transistors in a test circuit on a breadboard. Each device is then measured with a multimeter to read its gate/source cutoff voltage. This is the measurement you want to match with another transistor. The goal is to find two transistors whose V_{GS} are within just a couple of percent of one another. The closer the match, the better response one gets in the phase circuit. For the 2n5952 (or similarly the 2n5457) the best results tend to come from devices with a V_{GS} of -1.5 to -3.0V.

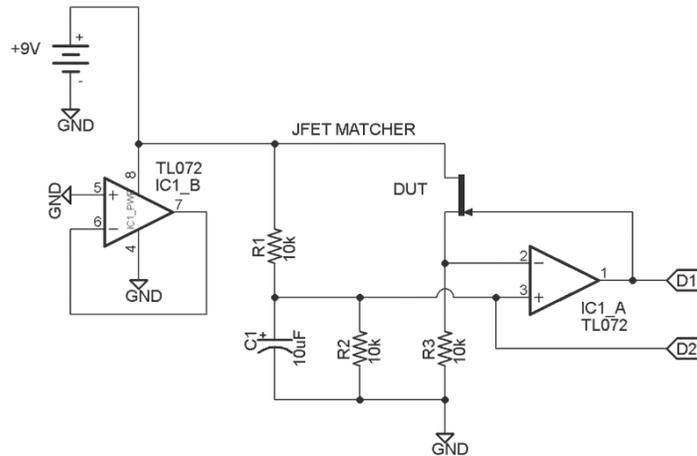

- You can put this testing circuit on a breadboard in about 5 minutes. Use the probes on your multimeter (set for DC voltage) to test the V_{GS} of each JFET at D1 and D2 testing point. V_{GS} values between -1v and -4v are typical. Try to match two transistors to one or two decimal places. Ex. -1.55v, etc). More info about matching JFETs for phase shifters can be found on the DIYStompboxes forum and R.G. Keen's website: http://www.geofex.com/article_folders/fetmatch/fetmatch.htm
- NOTE: You can also use 2n2457 if you can match them with a similar spec as described above. However, their pinouts are reversed from the 2n5952. The J201 has a much more narrow range of V_{GS} where they will work in phasers, so they are not recommended.

Biasing the phaser section

- Set the Speed control about halfway up. Start with the BIAS trim full CCW and adjust CW until you hear the phase effect. Adjust the Speed control and fine tune the BIAS trim for the most depth of phase attainable. NOTE: this can be a very narrow range on a single turn trimpot, so it may take a couple of tries. Use a multi-turn if you want more precision.

Voice Switch

- This version of the Smoothie includes a switch to toggle between different sets of caps for the two phase stages. The primary set are two 47n (C3 and C5) and the alternate set are a 10n and 100n (C2 and C4). This is the typical "Univibe" mod for the Phase 45. It is a pretty subtle difference, but worthy of the mod. You are free to experiment with alternate sets to get different phase tones. Socket C2 and C4 for experimentation.

Circuit Voltages

IC1	TL072	IC2	TL072
1	3.55	1	3.56
2	5.57	2	3.56
3	3.56	3	3.41
4	0	4	0
5	varies	5	3.56
6	varies	6	3.57
7	varies	7	3.58
8	9.25	8	9.25


9.44vDC One Spot supply
Current Draw: ~4mA

- Speed at 0, switch down.

1590B Drill Template

Coordinates are denoted in (X,Y), drill size format starting from the center (0,0) location of the enclosure.

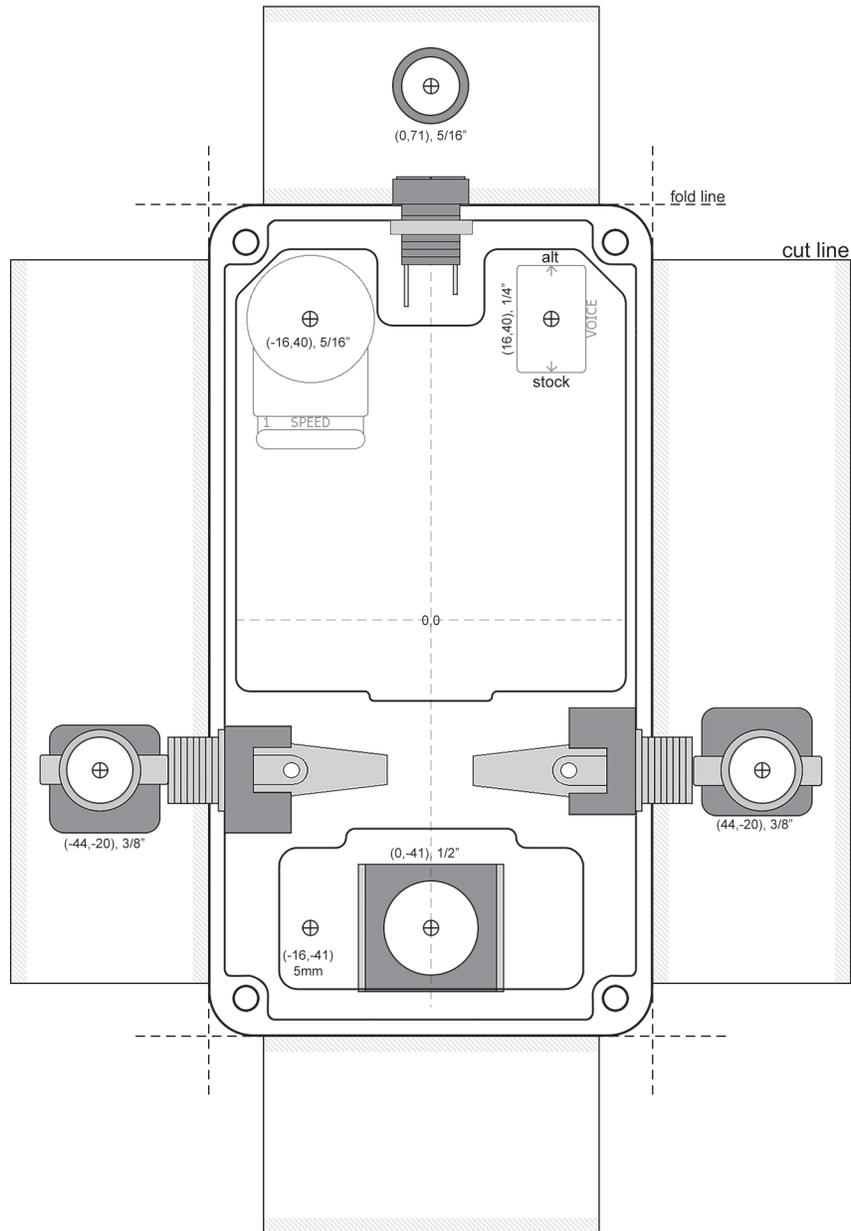[Link to Tayda Standard Series master drill template](#)




Hardware

1590B enclosure
Lumberg 1/4" Compact mono jacks
Slim 2.1mm DC jack
Standard 3PDT footswitch
5mm LED

NOTE: Different 1/4" and DC jack styles may require different sized drill holes.

Build Pic

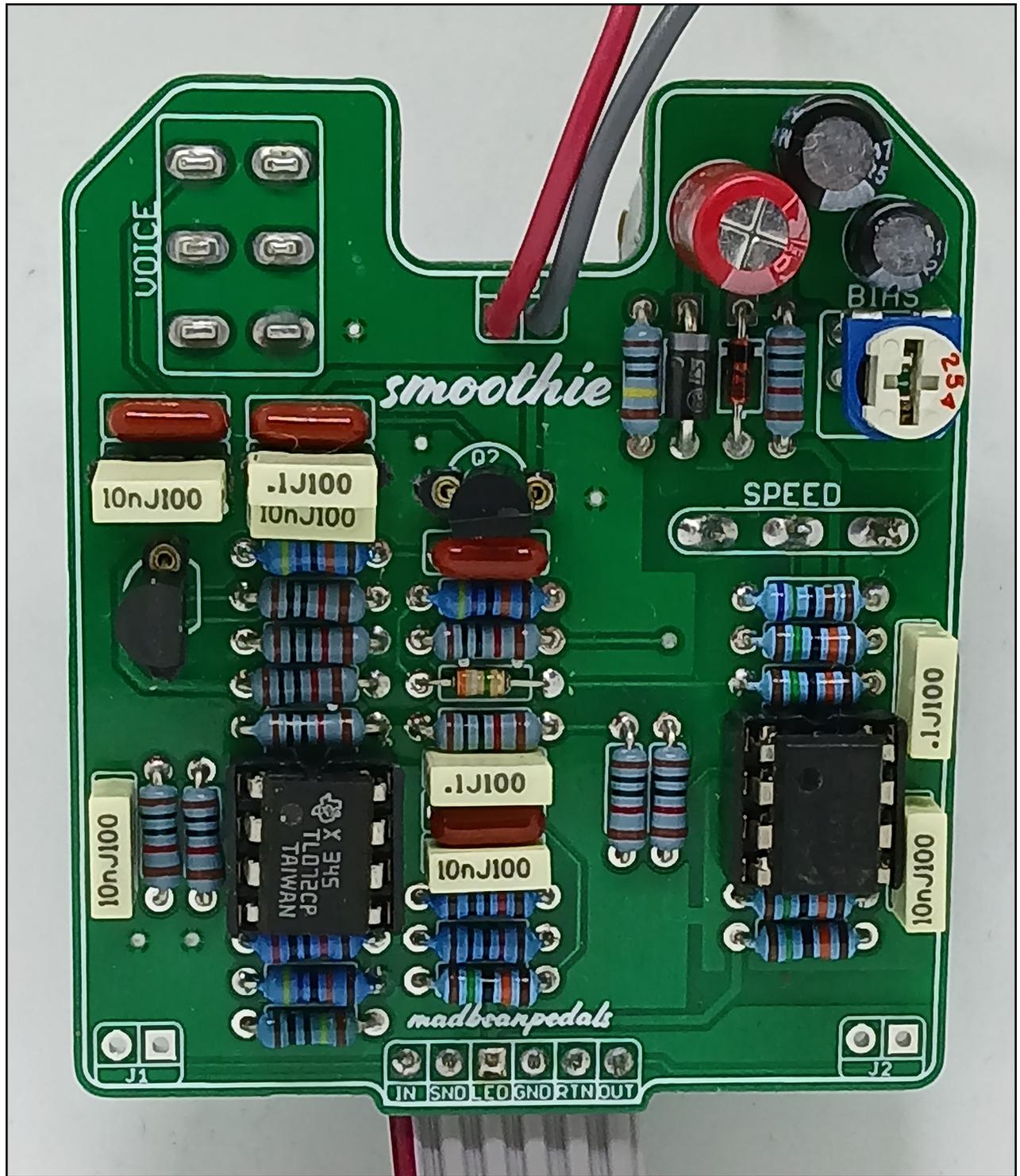

Schematic

